

# Linear voltage controller


## 1. Objectives

The purpose of this exercise is to learn the properties of a linear voltage regulator built on a common integrated circuit. The scope of the exercise includes the design and measurement of the basic parameters and characteristics of the stabilizer.

## 2. Components and instrumentation.

In Fig.1 the schematic diagram of the voltage regulator in the form of the basic L200 integrated circuit application is presented. Table 1 shows the basic parameters of the L200 stabilizer

a)

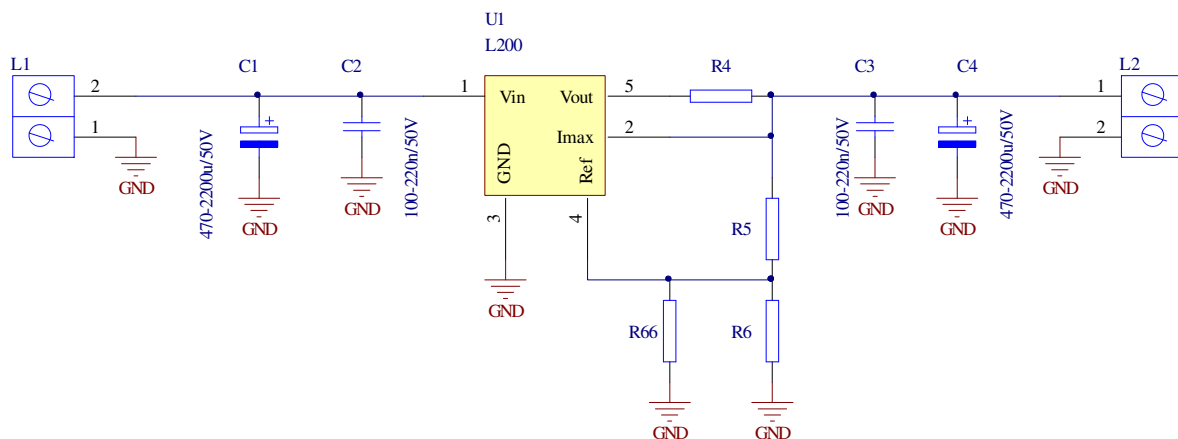

b)

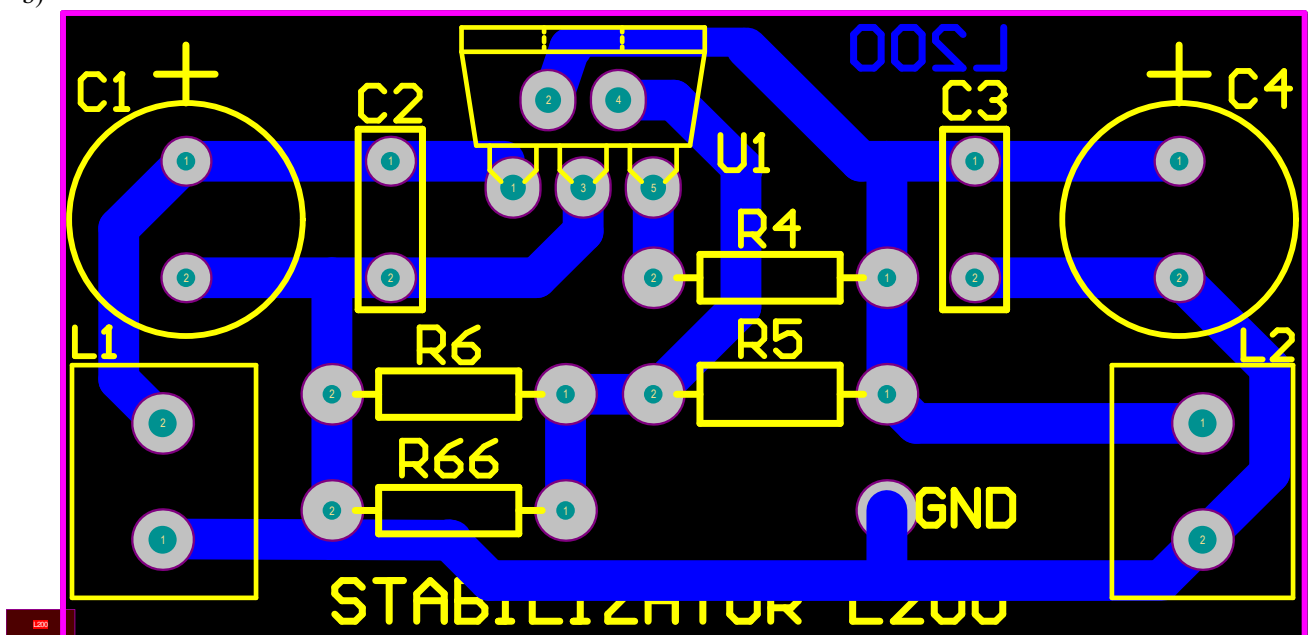


Fig. 1. Linear voltage regulator with current limit - application of IC L200; a) schematic diagram, b) PCB - element side view.

Table 1 Basic parameters of L200 integrated circuit

Symbol	Parametr	Conditions	alue			Unit.
			Min	Typ	Max	
<b>Voltage regulator T = 25°C</b>						
$U_O$	Input voltage range	$I_O = 10\text{mA}$	2.85	<>	36	V
$\Delta U_O/I_O$	Load regulation	$I_{\min} = 10\text{mA}$ $I_{\max} = 1,5\text{A}$	0.1	0.15	1	%
$\Delta U_O/\Delta U_I$	Line regulation	$U_I = 8\dots 20\text{V}$ $U_O = 5\text{V}$		0.1	0.4	%
$U_O - U_{I\min}$	Dropout voltage	$I_O = 1.5\text{A}$	2	2.5	3	V
$r_{out}$	Output impedance	$U_I = 10\text{V}, U_O = U_{REF}$ $I_O = 500\text{mA}$ $F = 100\text{Hz}$	1.5	1.5	3	mΩ
$U_{REF}$	Reference voltage	$U_I = 20\text{V},$ $I_O = 10\text{mA}$	2.65	2.75	2.85	V
<b>Current regulator T = 25°C</b>						
$U_{SC}$	Current limit sens voltage (pins 2 and 5)	$U_I = 10\text{V}, U_O = U_{REF}$ $I_O = 100\text{mA}$	0.38	0.45	0.52	V
$I_{SC}$	Peak short circuit current	$U_I - U_O = 14\text{V}$ (pomiędzy pin 2 i 5 włączono $R_{SC} < 0.01\Omega$ )			3.5	A
$\Delta I_O/I_O$	Current load regulation	$U_I = 10\text{V}, U_O = 3\text{V}$ $I_O = 0.5\text{A}$ $I_O = 1\text{A}$ $I_O = 1.5\text{A}$		1,4 1,0 0,9		%

The output voltage  $U_O$  of the regulator depends on the value of resistors  $R_5$  and  $R_6$  and can be calculated according to the equation:

$$U_O = \left(1 + \frac{R_5}{R_6}\right) U_{REF} \quad (1)$$

The output voltage can take values within the range  $U_{REF} < U_O < (U_I - U_{REF} - U_{BE})$ , where the  $U_{REF}$  is the reference voltage of the L200 circuit (between pins 3 and 4, so on the resistor  $R_6$  - typically 2.75V) and the  $U_{BE}$  is the voltage Base-Emitter of the transistor regulator included in the structure of the circuit. The maximum output current in the system is limited to the value:

$$I_{O\max} = \frac{U_{SC}}{R_4} = \frac{0,45\text{V}}{R_4} \quad (2)$$

so it is determined by the value of the  $R_4$  shunt resistor. The design of the stabilizer is reduced to the ratio of  $R_5/R_6$  according to (1), and the sum of the resistances  $R_5 + R_6$ , which will allow them to determine their specific values. These resistors should be selected in such a way that the current through the divider  $R_5$  and  $R_6$  is much higher than the polarity of the tip 4 ( $I_4$ ), which is a maximum of  $10\mu\text{A}$ . In practice you can accept

$$R_5 + R_6 \leq \frac{U_O}{100I_4} \approx \frac{U_O}{1\text{mA}} \quad (3)$$

### 3. Preparation.

NOTICE: The preparation time for classes is estimated at 4 to 6 hours.

### 3.1. Readings

- [1] Lab materials and lectures of the course.
- [2] U. Tietze, Ch. Schenk, Electronic circuits. Handbook for Design and Applications, Springer, 2008, p. 885-892.
- [3] P. Horowitz, W. Hill, The Art of Electronics, Cambridge Univ. Press, London, 2015,

### 3.2. Problems

1. Block diagram and principle of operation of the compensating voltage stabilizer.
2. Name and describe the basic parameters and characteristics of the voltage regulator.
3. Draw examples schematics of voltage regulator circuits.
4. List and describe the basic types of protections used in compensating stabilizers.
5. Integrated circuit L200: construction, operation, parameters and applications.
6. Describe the principles of voltage stabilizer design using the L200 chip.

### 3.3. Detailed preparation

For the given output voltage and the maximum output current of the voltage regulator, calculate and select elements R4, R5, R6. Prepare appropriate tables for the measurement results and graphs on which the characteristics will be plotted.

## 4. Contest of the report

### 4.1. Relationship $U_O = f(U_I)$ measurement, for $R_O$ as parameter

1. Assemble the designed voltage stabilizer on the PCB and attach the heatsink to the L200..
2. Connect the DC power supply to the regulator input and adjust the load in series with the ammeter. Connect voltmeters to the input and output (fig.2).

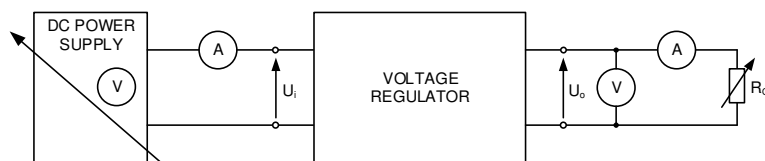


Fig.2. Measurement diagram.

3. Measure and plot the relationship  $U_O = f(U_I)$  for given  $R_O$  load resistance values.
4. Estimate the  $\Delta U_O$  stability ranges for the given load resistance and calculate the stabilization coefficients  $S_U$ ,

$$S_U = \frac{\Delta U_O}{\Delta U_I} \quad (4)$$

5. Specify the “Dropout” voltage stabilizer for given  $R_O$  resistance values.

#### 4.2. Relationship $U_O = f(I_O)$ measurement with, $U_I$ as parameter

6. Measure and plot the relationship  $U_O = f(I_O)$ , for given value of input voltage  $U_I$ . Measurements should be performed by changing the load resistance value from the unloaded state ( $R_O = \infty$ ) to the shorted state ( $R_O = 0$ ).
7. Determine the output voltage stabilization range  $\Delta U_O$  and the value of the output resistivity of the regulator  $R_{out}$ .

#### 4.3. Reference voltage measurement

8. Using a voltmeter, measure the reference voltage of the regulator -  $U_{REF}$  - voltage drop on  $R_6$ . Take the measurement with unloaded stabilizer ( $R_O = \infty$ ).
9. Using a voltmeter, measure the current limit sense voltage USC - voltage drop on  $R_4$ . Take the measurement when output is shorted ( $R_O = 0$ ).

## 4. Conclusions

1. Determine the effect of  $R_O$  on the relationship  $U_O = f(U_I)$ .
2. Determine the effect of  $U_I$  on the relationship  $U_O = f(I_O)$ .
3. Determine and interpret the values of the stabilization factor  $S_U$  and the output resistivity of the regulator.
4. For what value  $R_O$  and  $U_I$  the regulator works as a voltage regulator and for what values as a current regulator ?
5. Compare measured results with the stabilizer catalog data of L200 ic.

## 5. Appendixes:

№0.	Line regulation $U_o = f(U_I)$					
	$R_o = \dots\dots\Omega,$		$R_o = \dots\dots\Omega,$		$R_o = \dots\dots\Omega,$	
	$S_U = \dots\dots\dots V/V$		$S_U = \dots\dots\dots V/V$		$S_U = \dots\dots\dots V/V$	
	$U_o$ [V]	$U_I$ [V]	$U_o$ [V]	$U_I$ [V]	$U_o$ [V]	$U_I$ [V]
1.						
2.						
3.						
4.						
5.						
6.						
7.						
8.						
9.						
10.						
11.						
12.						
13.						
14.						
15.						
16.						
17.						
18.						
19.						
20.						
21.						
22.						

№.	Load regulation $U_o = f(I_o)$					
	$U_I = \dots\dots\dots\text{V}$		$U_I = \dots\dots\dots\text{V}$		$U_I = \dots\dots\dots\text{V}$	
	$r_{out} = \dots\dots\dots\Omega$		$r_{out} = \dots\dots\dots\Omega$		$r_{out} = \dots\dots\dots\Omega$	
	$U_o$ [V]	$I_o$ [mA]	$U_o$ [V]	$I_o$ [mA]	$U_o$ [V]	$I_o$ [mA]
1.						
2.						
3.						
4.						
5.						
6.						
7.						
8.						
9.						
10.						
11.						
12.						
13.						
14.						
15.						
16.						
17.						
18.						
19.						
20.						
21.						
22.						